

# ECE4700J Lab 1

## Verilog: Hardware Description Language

Haoyang Zhang

UM-SJTU Joint Institute

*zhy-sjtu-jc@sjtu.edu.cn*

May 18, 2022

# Overview

- 1 EECS 4700J
- 2 Verilog
- 3 Testing
- 4 Vivado Usage

# What?

- Lab 1 - Lab 3: SystemVerilog Design Tutorial and Environment Setup
- Lab 4: Introduction to RISC-V ISA and Pipeline
- Lab 5: Introduction to Chisel Language
- Lab 6: Introduction to Gem5 Simulator

# Where? When?

- Due to the completely online nature
  - Lab assignments will be released shortly before the start of the first lab each week.
  - A recording of the lab will be released after the lab lecture.
  - Please refer to the slides and recording for demonstrations and tips!
- Lab attendance is optional but strongly recommended!
  - Lab lectures will be at Thursday 10:00 am to 11:30 am (Beijing Time).
  - The first three Lab assignments must be checked off during a live meeting with the TA (Lab live demo). They are scheduled on Friday 8:00 pm - 10:00 pm (Beijing Time) of the week after they are assigned.
  - Labs are due by the end of lab the week after they are assigned.

- ECE4700J Piazza (Recommended)
  - Most of your lab/project related questions should be asked here so that other people can benefit from the answer.
  - Reminder: Please do not post program code in public questions.
- ECE4700J OH: on Friday 8:00 pm - 9:00 pm Beijing Time. (First 3 OHs can be used for live demo)
- ECE4700J Staff Email

# Lab Assignments

- All lab assignments are individual assignments.
  - Lab1 - Simple Arbitor Design (10%)
  - Lab2 - Some Verilog Debugging (10%)
  - Lab3 - A Pipelined Integer Square Root Module (15%)
  - Lab4 - RISCv Five-Stage Pipeline Optimization (30%)
  - Lab5 - FIFO and CAM Design (15%)
  - Lab6 - Gem5 Simulation of Spectre V1 Attack (20%)
- Some lab assignments also contain optional assignments. If you implement them correctly, you can get up to 10% bonus points to the total score of lab assignments.

- These lab assignments will take a non-trivial amount of time, especially if you're not a Verilog guru.
- You should start them early. Seriously...

- Lab 1 is due Friday 11:59pm May 27th, 2022 (Beijing Time)



## What is Verilog?

- ▶ Hardware Description Language - IEEE 1364-2005
  - ▶ Superseded by SystemVerilog - IEEE 1800-2009
- ▶ Two Forms
  1. Behavioral
  2. Structural
- ▶ It can be built into hardware. If you can't think of at least one (inefficient) way to build it, it might not be good.

## Why do I care?

- ▶ We use Behavioral Verilog to do computer architecture here.
- ▶ Semiconductor Industry Standard (VHDL is also common, more so in Europe)

# Verilog to SystemVerilog

- wire - wire/logic
- reg - logic
- always (\*) - always\_comb
- always (posedge clock) - always\_ff @(posedge clock)
- More on SystemVerilog later...

# The Difference Between Behavioral and Structural Verilog

## Behavioral Verilog

- ▶ Describes function of design
- ▶ Abstractions
  - ▶ Arithmetic operations  
(+, -, \*, /)
  - ▶ Logical operations  
(&, |, ^, ~)

## Structural Verilog

- ▶ Describes construction of design
- ▶ No abstraction
- ▶ Uses modules, corresponding to physical devices, for everything

Suppose we want to build an adder?

# Structural Verilog by Example

 


Figure: 1-bit Full Adder

# Structural Verilog by Example

---

```
module one_bit_adder(  
    input wire a,b,cin,  
    output wire sum,cout);  
    wire w_0,w_1,w_2;  
    xor u0(w_0,a,b);  
    xor u1(sum,w_0,cin);  
    and u2(w_1,w_0,cin);  
    and u3(w_2,a,b);  
    or u4(cout,w_1,w_2);  
endmodule
```

---

# Behavioral Verilog by Example

---

```
module one_bit_adder(  
    input wire a,b,cin,  
    output wire sum,cout);  
    assign sum = a ^ b ^ cin;  
    assign cout = ((a ^ b) & cin) | a & b;  
endmodule
```

---

# Behavioral Verilog by Example

---

```
module one_bit_adder(  
    input logic a,b,cin,  
    output logic sum,cout);  
  
    always_comb  
    begin  
        sum = a ^ b ^ cin;  
        cout = 1'b0;  
        if ((a ^ b) & cin) | (a & b))  
            cout = 1'b1;  
    end  
endmodule
```

---

Given specific hardware modules library, the process that changes the behavioral Verilog into fully structural Verilog.



## Synthesizable Data Types

`wires` Also called nets

---

```
wire a_wire;  
wire [3:0] another_4bit_wire;
```

---

- ▶ Cannot hold state

`logic` Replaced reg in SystemVerilog

---

```
logic [7:0] an_8bit_register;  
reg a_register;
```

---

- ▶ Holds state, might turn into flip-flops
- ▶ Less confusing than using reg with combinational logic (coming up. . .)

## Unsynthesizable Data Types

`integer` Signed 32-bit variable

`time` Unsigned 64-bit variable

`real` Double-precision floating point variable

# Types of Values

## Four State Logic

- 0 False, low
- 1 True, high
- Z High-impedance, unconnected net
- X Unknown, invalid, don't care

## Literals/Constants

- ▶ Written in the format <bitwidth>'<base><constant>
- ▶ Options for <base> are...
  - b Binary
  - o Octal
  - d Decimal
  - h Hexadecimal

---

```
assign an_8bit_register = 8'b10101111;  
assign a_32bit_wire = 32'hABCD_EF01;  
assign a_4bit_logic = 4'hE;
```

---

# Verilog Operators

Arithmetic	
*	Multiplication
/	Division
+	Addition
-	Subtraction
%	Modulus
**	Exponentiation
Bitwise	
~	Complement
&	And
	Or
~	Nor
^	Xor
^^	Xnor
Logical	
!	Complement
&&	And
	Or

Shift	
>>	Logical right shift
<<	Logical left shift
>>>	Arithmetic right shift
<<<	Arithmetic left shift
Relational	
>	Greater than
>=	Greater than or equal to
<	Less than
<=	Less than or equal to
!=	Inequality
!==	4-state inequality
==	Equality
===	4-state equality
Special	
{,}	Concatenation
{n{m}}	Replication
?:	Ternary

# Setting Values

## assign Statements

- ▶ One line descriptions of combinational logic
- ▶ Left hand side must be a wire (SystemVerilog allows assign statements on logic type)
- ▶ Right hand side can be any one line verilog expression
- ▶ Including (possibly nested) ternary (?:)

## Example

---

```
module one_bit_adder(  
    input wire a,b,cin,  
    output wire sum,cout);  
    assign sum = a ^ b ^ cin;  
    assign cout = ((a ^ b) & cin) | a & b;  
endmodule
```

---

## always Blocks

- ▶ Contents of always blocks are executed whenever anything in the sensitivity list happens
- ▶ Two main types in this class...
  - ▶ always\_comb
    - ▶ implied sensitivity lists of every signal inside the block
    - ▶ Used for combinational logic. Replaced always @\*
  - ▶ always\_ff @(posedge clk)
    - ▶ sensitivity list containing only the positive transition of the clk signal
    - ▶ Used for sequential logic
- ▶ All left hand side signals need to be logic type.

# Always Block Examples

## Combinational Block

```
always_comb
begin
    x = a + b;
    y = x + 8'h5;
end
```

## Sequential Block

```
always_ff @(posedge clk)
begin
    x <= #1 next_x;
    y <= #1 next_y;
end
```



# Blocking vs. Nonblocking Assignments

## Blocking Assignment

- ▶ Combinational Blocks
- ▶ Each assignment is processed in order, earlier assignments block later ones
- ▶ Uses the = operator

vs.

## Nonblocking Assignment

- ▶ Sequential Blocks
- ▶ All assignments occur “simultaneously,” delays are necessary for accurate simulation
- ▶ Uses the <= operator

# Blocking vs. Nonblocking Assignments by Example

## Blocking Example

```
always_comb
begin
    x = new_val1;
    y = new_val2;
    sum = x + y;
end
```

- ▶ Behave exactly as expected
- ▶ Standard combinational logic

 


Figure: Timing diagram for the above example.

# Blocking vs. Nonblocking Assignments by Example

## Nonblocking Example

```
always_ff @(posedge clock)
begin
    x <= #1 new_val1;
    y <= #1 new_val2;
    sum <= #1 x + y;
end
```

- ▶ What changes between these two examples?
- ▶ Nonblocking means that sum lags a cycle behind the other two signals

 


Figure: Timing diagram for the above example.

# Blocking vs. Nonblocking Assignments by Example

## Bad Example

```
always_ff @(posedge clock)
begin
    x <= #1 y;
    z = x;
end
```

- ▶ z is updated after x
- ▶ z updates on negedge clock

 


Figure: Timing diagram for the above example.

## Latches

- ▶ What is a latch?
  - ▶ Memory device without a clock
- ▶ Generated by a synthesis tool when a net needs to hold state without being clocked (combinational logic)
- ▶ Generally bad, unless designed in intentionally
- ▶ Unnecessary in this class

## Latches

- ▶ Always assign every variable on every path
- ▶ This code generates a latch
- ▶ Why does this happen?

---

```
always_comb
begin
    if (cond)
        next_x = y;
end
```

---

## Possible Solutions to Latches

---

```
always_comb
begin
    next_x = x;
    if (cond)
        next_x = y;
end
```

---

```
always_comb
begin
    if (cond)
        next_x = y;
    else
        next_x = x;
end
```

---

## Intro to Modules

- ▶ Basic organizational unit in Verilog
- ▶ Can be reused

## Module Example

---

```
module my_simple_mux(  
    input wire select_in, a_in, b_in; //inputs listed  
    output wire muxed_out); //outputs listed  
    assign muxed_out = select_in ? b_in : a_in;  
endmodule
```

---



## Writing Modules

- ▶ Inputs and outputs must be listed, including size and type  
format: <dir> <type> <[WIDTH-1:0]> <name>;  
e.g. output logic [31:0] addr;
- ▶ In module declaration line or after it, inside the module

## Instantiating Modules

- ▶ Two methods of instantiation
  1. e.g. `my_simple_mux m1(.a_in(a),.b_in(b),  
  .select_in(s),.muxed_out(m));`
  2. e.g. `my_simple_mux m1(a,b,s,m);`
- ▶ The former is much safer...
- ▶ Introspection (in testbenches): `module.submodule.signal`

# How to Design with Verilog

- ▶ Remember – Behavioral Verilog implies no specific hardware design
- ▶ But, it has to be synthesizable
- ▶ Better be able to build it somehow

## Combinational Logic

- ▶ Avoid feedback (combinatorial loops)
- ▶ Always blocks should
  - ▶ Be `always_comb` blocks
  - ▶ Use the blocking assignment operator `=`
- ▶ All variables assigned on all paths
  - ▶ Default values
  - ▶ `if(...)` paired with an `else`

## Sequential Logic

- ▶ Avoid clock- and reset-gating
- ▶ Always blocks should
  - ▶ Be `always_ff @(posedge clock) blocks`
  - ▶ Use the nonblocking assignment operator, with a delay `<= #1`
- ▶ No path should set a variable more than once
- ▶ Reset all variables used in the block
- ▶ `//synopsys sync_set_reset "reset"`

## All Flow Control

- ▶ Can only be used inside procedural blocks (always, initial, task, function)
- ▶ Encapsulate multiline assignments with `begin...end`
- ▶ Remember to assign on all paths

## Synthesizable Flow Control

- ▶ `if/else`
- ▶ `case`

## Unsynthesizable Flow Control

- ▶ Useful in testbenches
- ▶ For example...
  - ▶ `for`
  - ▶ `while`
  - ▶ `repeat`
  - ▶ `forever`

# Flow Control by Example

## Synthesizable Flow Control Example

---

```
always_comb
begin
    if (muxy == 1'b0)
        y = a;
    else
        y = b;
end
```

---

## The Ternary Alternative

---

```
wire y;
assign y = muxy ? b : a;
```

---

## What is a test bench?

- ▶ Provides inputs to one or more modules
- ▶ Checks that corresponding output makes sense
- ▶ Basic building block of Verilog testing

## Why do I care?

- ▶ Finding bugs in a single module is hard...
- ▶ But not as hard as finding bugs after combining many modules
- ▶ Better test benches tend to result in higher project scores



## Features of the Test Bench

- ▶ Unsynchronized
  - ▶ Remember unsynthesizable constructs? This is where they're used.
  - ▶ In particular, unsynthesizable flow control is useful in testbenches (e.g. `for`, `while`)
- ▶ Programmatic
  - ▶ Many programmatic, rather than hardware design, features are available e.g. functions, tasks, classes (in SystemVerilog)

# Anatomy of a Test Bench

A good test bench should, in order...

1. Declare inputs and outputs for the module(s) being tested
2. Instantiate the module (possibly under the name DUT for Device Under Test)
3. Setup a clock driver (if necessary)
4. Setup a correctness checking function (if necessary/possible)
5. Inside an `initial` block...
  - 5.1 Assign default values to all inputs, including asserting any available reset signal
  - 5.2 `$monitor` or `$display` important signals
  - 5.3 Describe changes in input, using good testing practice

# Unsynthesizable Procedural Blocks

## `initial` Blocks

- ▶ Procedural blocks, just like always
- ▶ Contents are simulated once at the beginning of a simulation
- ▶ Used to set values inside a test bench
- ▶ Should only be used in test benches

## initial Block Example

---

```
initial
begin
    @(negedge clock);
    reset = 1'b1;
    in0 = 1'b0;
    in1 = 1'b1;
    @(negedge clock);
    reset = 1'b0;
    @(negedge clock);
    in0 = 1'b1;
    ...
end
```

---

# List of System Tasks and Functions

- `$monitor` Used in test benches. Prints every time an argument changes. Very bad for large projects.  
e.g. `$monitor("format",signal,...)`
- `$display` Can be used in either test benches or design, but not after synthesis. Prints once. Not the best debugging technique for significant projects.  
e.g. `$display("format",signal,...)`
- `$strobe` Like display, but prints at the end of the current simulation time unit.  
e.g. `$strobe("format",signal,...)`
- `$time` The current simulation time as a 64 bit integer.
- `$reset` Resets the simulation to the beginning.
- `$finish` Exit the simulator, return to terminal.

# Test Benches by Example

## Test Bench Setup

---

```
module testbench;  
    logic clock, reset, taken, transition, prediction;  
  
    two_bit_predictor(  
        .clock(clock),  
        .reset(reset),  
        .taken(taken),  
        .transition(transition),  
        .prediction(prediction));  
  
    always  
    begin  
        clock = #5 ~clock;  
    end
```

---

# Test Benches by Example

## Test Bench Test Cases

---

```
initial
begin
    $monitor("Time:%4.0f clock:%b reset:%b taken:%b trans:%b"
             "pred:%b", $time, clock, reset, taken,
             transition, prediction);
    clock = 1'b1;
    reset = 1'b1;
    taken = 1'b1;
    transition = 1'b1;
    @(negedge clock);
    @(negedge clock);
    reset = 1'b0;
    @(negedge clock);
    taken = 1'b1;
    @(negedge clock);
    ...
    $finish;
end
```

# Test Benches Tips

Remember to...

- ▶ Initialize all module inputs
- ▶ Then assert reset
- ▶ Use `@(negedge clock)` when changing inputs to avoid race conditions



- Learn to see Vivado Synthesis Reports
- Avoid Latch
- Avoid timing violation
- Demo



Jon Beaumont (2021)

EECS470 Lab1

# Thanks